

Op - 15 / 2023

Ej. Tenemos la siguiente expresión algebraica lógica


$$M = AB + C\bar{D} + \bar{A}D + \bar{C}B$$

- a) Expandir en la forma estándar de productos de suma la expresión M.
- b) Simplificar usando solamente algebra de Boole.

Dibujar el circuito lógico obtenido en (A) y (B)

Ej. Se tiene cuatro electroválvulas para controlar los flujos de agua de un sistema de tuberías. los flujos a través de cada una de las electroválvulas son 10, 15, 25, 45, respectivamente.

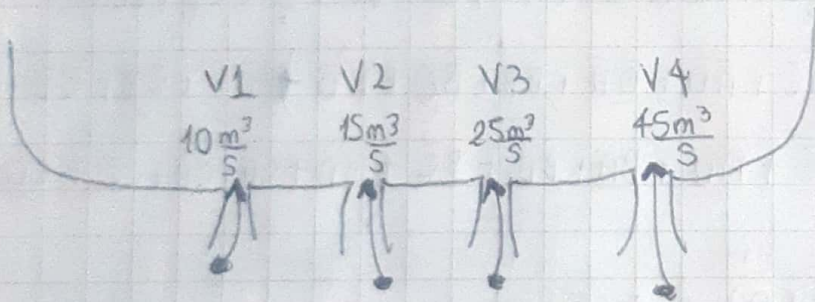$(\frac{m^3}{seg})$
 $(\frac{m^3}{s})$
 $(l / tiempo)$



- a) obtener la tabla de la verdad para ofrecer a la salida del sistema hidráulico : $10 \frac{m^3}{s}$, $40 \frac{m^3}{s}$, $85 \frac{m^3}{s}$, $60 \frac{m^3}{s}$, $35 \frac{m^3}{s}$, $70 \frac{m^3}{s}$
- b) Determine la expresión lógica de salida en su forma estándar de productos de suma.
- c) Obtener la expresión lógica mínima usando MR.
- d) Dibujar exp. alg. lógica obtenida en el ítem c)

Series

$$A + AB = A + B$$

$$A + A\bar{B}$$

$$AC + AC = AC$$

$$A(B+B) =$$

①

$$H = AB + C\bar{D} + \bar{A}D + \bar{C}B$$

• Primero expandimos: (en productos de sumas)

$A B \bar{C} D$	$A B C \bar{D}$	$\bar{A} B C D$	$A B \bar{C} \bar{D}$
$A B C D$	$A \bar{B} C \bar{D}$	$\bar{A} B \bar{C} D$	$A B C D$
$A B \bar{C} \bar{D}$	$A B C D$	$\bar{A} \bar{B} C D$	$A B \bar{C} D$
$A B C D$	$A \bar{B} C D$	$\bar{A} \bar{B} C \bar{D}$	$A B C \bar{D}$

a)

$$H = (A+B+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+B+C+\bar{D})(\bar{A}+\bar{B}+C+\bar{D})$$

$$(\bar{A}+B+C+D)(\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+\bar{C}+D)(\bar{A}+B+\bar{C}+D)$$

$$(A+B+C+\bar{D})(A+B+\bar{C}+\bar{D})(A+B+\bar{C}+D)(\bar{A}+B+\bar{C}+D)$$

b) Simplificar:

$$H = (A\bar{A} + A\bar{B} + A\bar{C} + A\bar{D} + BA + B\bar{B} + BC + B\bar{D} + CA + C\bar{B} + \bar{C}C + C\bar{D})$$

$$(A + \bar{B} + C + \bar{D})(A + B + C + D)$$

$$\bar{A}BC\bar{D} + A\bar{B}CD$$

Scribe
XOR

$$\begin{aligned}
 M &= (A + A(\bar{B} + B) + \overbrace{AC + AC}^{AC} + A(\bar{D} + D) + C(\bar{B} + B) + \overbrace{B\bar{D} + D\bar{B}}^{XOR} + C \\
 &+ C(\bar{D} + D)) \cdot (\bar{A} + \bar{A}(\bar{B} + B) + \overbrace{\bar{A}C + \bar{A}C}^{AC} + \overbrace{\bar{A}\bar{D} + \bar{A}D}^{XOR} + C(\bar{B} + B) + \bar{D}(\bar{B} + B) + C + \bar{D} \\
 &+ C\bar{D} + C\bar{D}) \cdot (\bar{A}(\bar{B} + B) + \bar{A} + \overbrace{\bar{A}C + \bar{A}C}^{AC} + \overbrace{\bar{A}D + \bar{A}D}^{XOR} + C(\bar{B} + B) + D(\bar{B} + B) + C \\
 &+ C\bar{D} + C\bar{D} + D\bar{D}) \cdot (\bar{A} + \bar{A}(\bar{B} + B) + \overbrace{\bar{A}\bar{C} + \bar{A}\bar{C}}^{AC} + \overbrace{\bar{A}(\bar{D} + D)}^{XOR} + \bar{C}(\bar{B} + B) + \overbrace{\bar{B}\bar{D} + B\bar{D}}^{XOR} + \bar{C} \\
 &+ \bar{C}(\bar{D} + D)) \cdot (A + \overbrace{AB + AB}^{XOR} + A(\bar{C} + C) + A(\bar{D} + D) + B + \overbrace{B(\bar{C} + C)}^{XOR} + B(\bar{D} + D) + 0 \\
 &+ CD + C\bar{D} + \bar{D}D) \cdot (0 + B(\bar{A} + A) + \bar{C}(\bar{A} + A) + AD + \bar{A}\bar{D} + B + \overbrace{B\bar{C} + B\bar{C}}^{XOR} + \bar{C} \\
 &+ B(\bar{D} + D) + \underbrace{\bar{C}D + C\bar{D}}_{XOR} + \bar{D}D)
 \end{aligned}$$

$$M = (A + A + AC + A + C + \overbrace{B\bar{D} + D\bar{B}}^{\text{XOR}} + C + C) \cdot (\bar{A} + \bar{A} + \bar{A}C + \bar{A}\bar{D} + C + \bar{D} + C + C\bar{D} + \bar{D}) \cdot (\bar{A} + \bar{A} + \bar{A}C + \bar{A}\bar{D} + C + D + C + C\bar{D} + D) \cdot (\bar{A} + \bar{A} + \bar{A}\bar{C} + \bar{A} + \bar{C} + \bar{B}\bar{D} + B\bar{D} + \bar{C} + \bar{C}) \cdot (A + AB + A + A + B + B + B + CD + \bar{C}\bar{D} + \bar{D}D) \cdot (B + \bar{C} + AD + \bar{A}\bar{D} + B + B\bar{C} + \bar{C} + B + \underbrace{\bar{C}D + C\bar{D}}_{\text{XOR}} + \bar{D}D)$$

$$M = (\overbrace{A + C + AC}^A + B \oplus D) \cdot (\bar{A} + C + \bar{D} + \bar{A}C + \bar{A}\bar{D} + C\bar{D}) \cdot (\bar{A} + C + D + \bar{A}C + \bar{A}\bar{D} + C\bar{D}) \cdot (\bar{A} + \bar{C} + \bar{A}\bar{C} + \bar{B}\bar{D} + B\bar{D}) \cdot (A + B + AB + CD + \bar{C}\bar{D} + \bar{D}D) \cdot (B + \bar{C} + AD + \bar{A}\bar{D} + \underbrace{B\bar{C} + \bar{C}D + C\bar{D} + \bar{D}D}_{\text{XOR}})$$

Reglas

$$\bar{A} + AB = A$$

$$A + \bar{A}B = A + B$$

$$A + BC = (A + B)(A + C)$$

$$M = (\overbrace{A + C}^{\bar{A}} + B \oplus D) \cdot (\overbrace{\bar{A} + \bar{A}C}^{\bar{A}} + \overbrace{\bar{D} + \bar{A}\bar{D}}^{\bar{D}} + \underbrace{C + C\bar{D}}_C) \cdot (\overbrace{\bar{A} + \bar{A}C}^{\bar{A}} + \overbrace{\bar{D} + \bar{A}\bar{D}}^{\bar{D}} + \underbrace{C + C\bar{D}}_C) \cdot (\overbrace{\bar{A} + \bar{A}\bar{C}}^{\bar{A}} + \overbrace{\bar{B}\bar{D} + B\bar{D}}^{\bar{B}}) \cdot (A + AB + B + CD + \bar{C}\bar{D} + \bar{D}D) \cdot (\underbrace{AD + \bar{A}\bar{D}}_{\bar{C}} + B + \underbrace{B\bar{C} + \bar{C}}_{\bar{C}} + \bar{D}D + C \oplus D)$$

$$\begin{aligned}
 M &= (A+C+B\oplus D) \cdot (\overline{A} + \overline{A}C + \overline{D} + \overline{A}\overline{D} + \underbrace{C + C\overline{D}}_C) \\
 &\cdot (\overline{A} + \overline{A}C + \overline{A}\overline{D} + \underbrace{D + C + C\overline{D}}_C) \cdot (\overline{A} + \overline{A}C + \overline{C} + \overline{B}\overline{D} + \underbrace{BD}_B) \cdot (A + AB + B + CD + \overline{C}\overline{D} + \overline{D}\overline{D}) \\
 &\cdot (\overline{A}\overline{D} + \overline{A}\overline{D} + B + \overline{B}\overline{C} + \overline{C} + \overline{D}\overline{D} + \underbrace{C\oplus D}_C)
 \end{aligned}$$

$$A + \overline{A}B = A + B$$

$$A + BC = (A+B)(A+C)$$

$$\hookrightarrow \text{Para } \overline{A} + \overline{A}C = \overline{A} \cdot 1 + \overline{A}C = \overline{A}(C + \overline{C}) + \overline{A}C = \overline{A}C + \overline{A}\overline{C} + \overline{A}C = \overline{A}\overline{C} + \overline{A}C = \overline{A}(C + \overline{C}) = \overline{A}$$

$$\hookrightarrow \text{Para } \overline{D} + \overline{A}\overline{D} = \overline{D} \cdot 1 + \overline{A}\overline{D} = \overline{D}(\overline{A} + A) + \overline{A}\overline{D} = \overline{D}\overline{A} + \overline{D}A + \overline{A}\overline{D} = \overline{D}(\overline{A} + \overline{A} + A) = \overline{D}(\overline{A} + A) = \overline{D}$$

$$\hookrightarrow \text{Para } C + C\overline{D} = C \cdot 1 + C\overline{D} = C(\overline{D} + D) + C\overline{D} = C\overline{D} + CD + C\overline{D} = C(\overline{D} + \overline{D} + D) = C$$

$$\hookrightarrow \text{Para } \overline{A} + \overline{A}C = \overline{A}(C + \overline{C} + C) = \overline{A}C$$

cambrá \bar{D}

$$M = (A + C + B \oplus D) \cdot (\bar{A} + \bar{D} + C) \cdot (\bar{A} + \bar{D} + C) \cdot (\bar{A} + \bar{C} + \overbrace{B\bar{D} + BD}^{\text{XNOR}})$$

$$\cdot (A + B + \underbrace{CD + \bar{C}\bar{D} + \bar{D}D}_{\text{XNOR}}) \cdot (\underbrace{AD + \bar{A}\bar{D}}_{\text{XNOR}} + B + \bar{C} + \bar{D}D + C \oplus D)$$

$$M = (A + C + B \oplus D) \cdot (\bar{A} + C) \cdot (\bar{A} + \bar{C} + \overline{B \oplus D}) \cdot (A + B + \overline{C \oplus D} + \bar{D}D) \cdot (\overline{A \oplus D} + B + \bar{C} + \bar{D}D + \overline{C \oplus D})$$

$$M = (A + C + B \oplus D) \cdot (\bar{A} + \bar{A}C + \bar{A}(\overline{B \oplus D}) + \bar{A}C + \bar{C} + \bar{C}(\overline{B \oplus D})) \cdot (A + B + \bar{D}D + \overline{C \oplus D})$$

$$(B + \bar{C} + \bar{D}D + \overline{A \oplus D} + C \oplus D)$$

$\bar{A}(1 + \bar{C})$

$$M = (A + C + B \oplus D) (\bar{A} + \bar{A}C + \bar{C} + \bar{C}(\overline{B \oplus D}) + \bar{A}(\overline{B \oplus D})) \cdot (A + B + \bar{D}D + \overline{C \oplus D})$$

$$(B + \bar{C} + \bar{D}D + \overline{A \oplus D} + C \oplus D)$$


$$M = (A + C + B \oplus D) \cdot (\bar{A} + \bar{C} + \bar{A}(\overline{B \oplus D}) + \bar{C}(\overline{B \oplus D})) \cdot (A + B + \bar{D}D + \overline{C \oplus D})$$

$$(B + \bar{C} + \bar{D}D + \overline{A \oplus D} + C \oplus D)$$

circuito lógico de a) $M = (A+B+C+D)(A+B+C+\bar{D})(A+B+C+\bar{D})(A+B+C+\bar{D})$

$(\bar{A}+B+C+D)(\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+\bar{C}+D)(\bar{A}+B+\bar{C}+\bar{D})(A+B+C+\bar{D})(A+B+\bar{C}+D)$

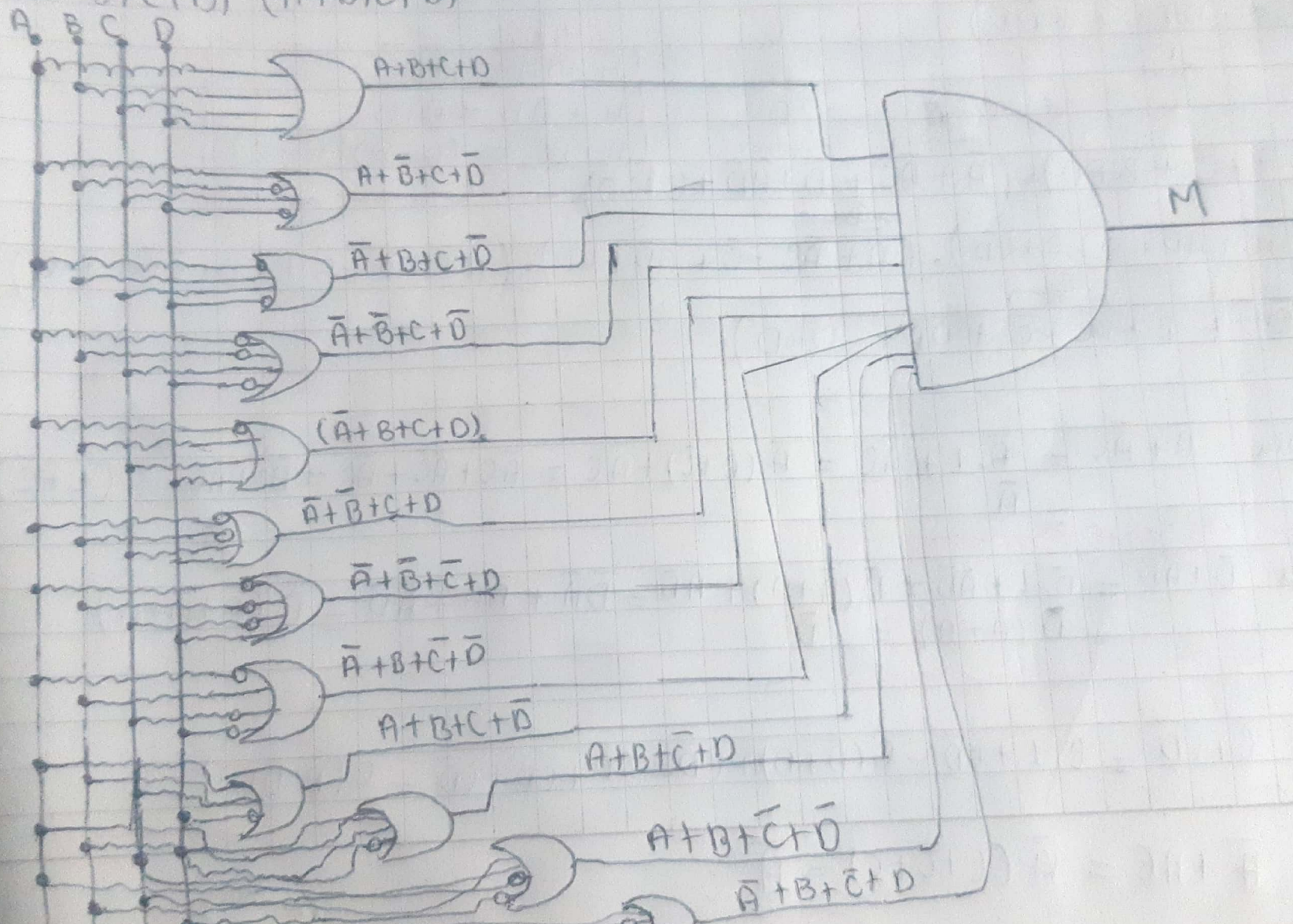
$(A+B+\bar{C}+\bar{D})(\bar{A}+B+\bar{C}+D)$



Circuito lógico de b)

Scribe
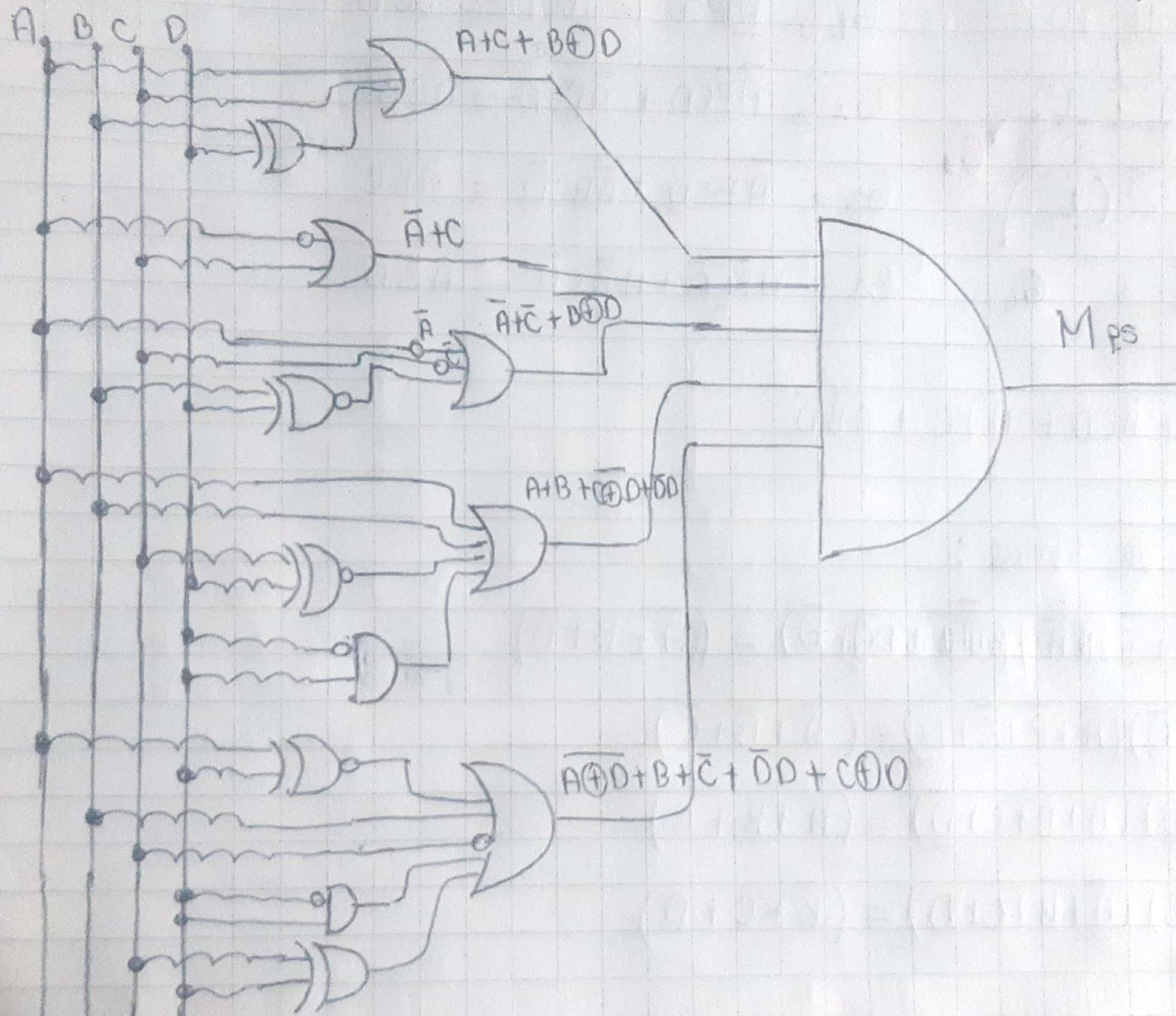
$$M = (A + C + B \oplus D) \cdot (\bar{A} + C) (\bar{A} + \bar{C} + \overline{B \oplus D}) \cdot (A + B + \overline{C \oplus D} + \bar{D}) \cdot (\overline{A \oplus D} + B + \bar{C} + \bar{D} + C \oplus D)$$



2) a)

	10	15	25	45	S	
A	B	C	D			
0	0	0	0	0		
0	0	0	1	0		
0	0	1	0	0		
0	0	1	1	1	$\rightarrow V_3 + V_4 = 25 + 45 = 70 \text{ m}^3/\text{s}$	(6)
0	1	0	0	0		
0	1	0	1	1	$\rightarrow V_2 + V_4 = 15 + 45 = 60 \text{ m}^3/\text{s}$	(4)
0	1	1	0	1	$\rightarrow V_2 + V_3 = 15 + 25 = 40 \text{ m}^3$	(2)
0	1	1	1	1	$\rightarrow V_2 + V_3 + V_4 = 15 + 25 + 45 = 85 \text{ m}^3/\text{s}$	(3)
1	0	0	0	1	$\rightarrow 10 \text{ m}^3/\text{s} : V_1$	(1)
1	0	0	1	0		
1	0	1	0	1	$\rightarrow V_1 + V_3 = 10 + 25 = 35 \text{ m}^3/\text{s}$	(5)
1	0	1	1	0		
1	1	0	0	0		
1	1	0	1	1	$\rightarrow V_1 + V_2 + V_4 = 10 + 15 + 45 = 70 \text{ m}^3/\text{s}$	(6)
1	1	1	0	0		
1	1	1	1	0		

$$\begin{array}{ll}
 0 & 1 & 0 & 0 & 1 & \rightarrow V_3 + V_4 = 25 + 45 = 70 \text{ m}^3/\text{s} \quad (6) \\
 0 & 1 & 0 & 1 & 1 & \rightarrow V_2 + V_4 = 15 + 45 = 60 \text{ m}^3/\text{s} \quad (4) \\
 0 & 1 & 1 & 0 & 1 & \rightarrow V_2 + V_3 = 15 + 25 = 40 \text{ m}^3 \quad (2) \\
 0 & 1 & 1 & 1 & 1 & \rightarrow V_2 + V_3 + V_4 = 15 + 25 + 45 = 85 \text{ m}^3/\text{s} \quad (3) \\
 1 & 0 & 0 & 0 & 1 & \rightarrow 10 \text{ m}^3/\text{s} : V_1 \quad (1) \\
 1 & 0 & 0 & 1 & 0 & \\
 1 & 0 & 1 & 0 & 1 & \rightarrow V_1 + V_3 = 10 + 25 = 35 \text{ m}^3/\text{s} \quad (5) \\
 1 & 0 & 1 & 1 & 0 & \\
 1 & 1 & 0 & 0 & 0 & \\
 1 & 1 & 0 & 1 & 1 & \rightarrow V_1 + V_2 + V_4 = 10 + 15 + 45 = 70 \text{ m}^3/\text{s} \quad (6) \\
 1 & 1 & 1 & 0 & 0 & \\
 1 & 1 & 1 & 1 & 0 &
 \end{array}$$

b) En productos de sumas :

$$S_{ps} = (A+B+C+D)(A+B+C+\bar{D})(A+B+\bar{C}+D)(A+\bar{B}+C+D)(\bar{A}+B+C+\bar{D})(\bar{A}+B+\bar{C}+\bar{D})(\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+\bar{C}+D)(\bar{A}+\bar{B}+\bar{C}+\bar{D})$$

C) M.K.:

AB \ CD	00	01	11	10
00	0	0	1	0
01	0	1	1	1
11	0	1	0	0
10	1	0	0	1

Diagram showing groupings for Karnaugh map simplification:

- G_1 : Group of 2 cells (00,1) and (01,1)
- G_2 : Group of 2 cells (01,1) and (11,1)
- G_3 : Group of 2 cells (11,1) and (11,0)
- G_4 : Group of 2 cells (00,1) and (10,1)
- G_5 : Group of 2 cells (01,1) and (11,0)
- G_6 : Group of 2 cells (11,0) and (10,1)
- G_7 : Group of 2 cells (00,1) and (00,0)
- G_8 : Group of 2 cells (00,0) and (10,0)
- G_9 : Group of 2 cells (10,0) and (10,1)

• En sumas de productos:

$$G_1 = \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}D = \bar{B}\bar{C}D$$

$$G_2 = \bar{A}\bar{B}CD + \bar{A}BCD = \bar{A}CD$$

$$G_3 = \bar{A}BCD + \bar{A}BC\bar{D} = \bar{A}BC$$

$$G_4 = A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} = A\bar{B}\bar{D}$$

$$\rightarrow S_{sp} = \bar{B}\bar{C}D + \bar{A}CD + \bar{A}BC + A\bar{B}\bar{D}$$

$$sp = \overline{C}D + A\overline{C}D + A\overline{B}C + A\overline{B}D$$

• En Productos de sumas:

$$\rightarrow G_5 = (\overline{A} + B + \underline{\overline{C}} + \overline{D})(\overline{A} + B + \underline{\overline{C}} + \overline{D}) = (\overline{A} + B + \overline{D})$$

$$\rightarrow G_6 = (\overline{A} + \overline{B} + \underline{\overline{C}} + \overline{D})(\overline{A} + \overline{B} + \underline{\overline{C}} + D) = (\overline{A} + \overline{B} + \overline{C})$$


$$G_7 = (A + B + C + \underline{D})(A + B + C + \underline{D}) = (A + B + C)$$

$$G_8 = (\underline{A} + \overline{B} + C + D)(\underline{A} + \overline{B} + C + D) = (\overline{B} + C + D)$$


$$G_9 = A + B + \overline{C} + D$$

$$Sps = (\overline{A} + B + \overline{D})(\overline{A} + \overline{B} + \overline{C})(A + B + C)(\overline{B} + C + D)(A + B + \overline{C} + D)$$
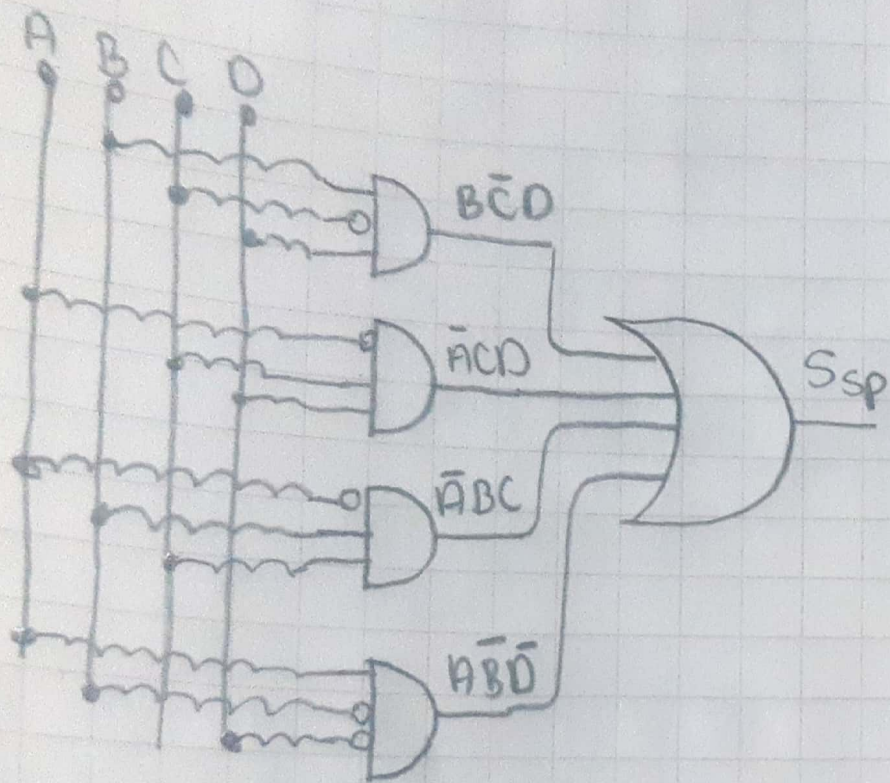
$$(A+B+C)(A+B+C)(\bar{B}+C+D)(A+B+\bar{C}+D)$$



En sumas de productos

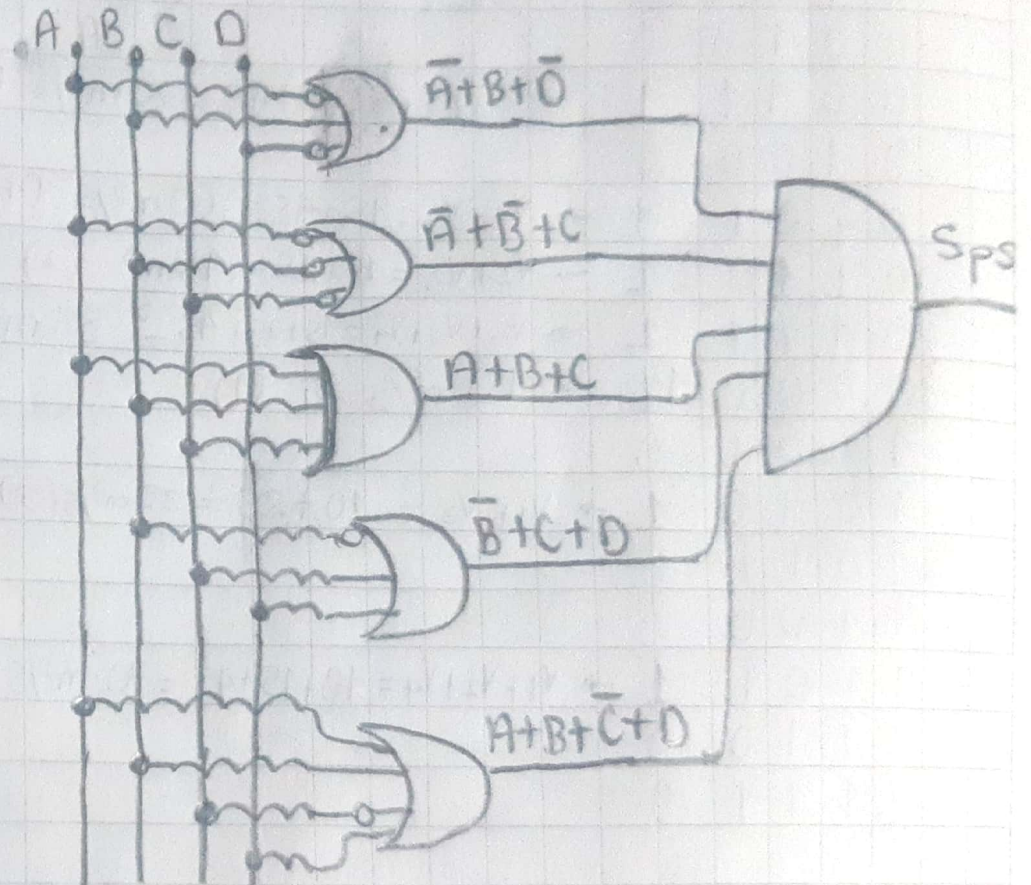

En productos de sumas